

ULTRA CAPACITORS INSTEAD OF BATTERIES.

VERY LIGHT, BUT NOT MUCH ENERGY.

SUPPOSE 50F CAPACITORS, & STRINGS OF 12 PAIRS OF 2 IN PARALLEL, 27A MAX CURRENT, THAT'S WHY NEED TWO,



$$\text{TOTAL CAPACITANCE} = \frac{50 \cdot 2}{12} = \frac{50}{6} = \frac{25}{3} = 8.3 \text{ F}$$

WORKING VOLTAGE 2.5V EACH CAP, SO FOR STRING, 30V

SUPPOSE DISCHARGE FROM 30V TO 20V.

$$E = \frac{1}{2} C V^2 \quad \text{AT } 30\text{V} = \frac{1}{2} C (30^2)$$
$$\quad \quad \quad \text{AT } 20\text{V} = \frac{1}{2} C (20^2)$$

$$\text{ENERGY AVAILABLE} = \frac{1}{2} \cdot 8.3 \cdot (900 - 400)$$
$$= 2075 \text{ J} \quad \text{2 SECONDS @ 1 KW.}$$

MAXWELL BCAP0050-P270 - 20% TOLERANCE. DON'T WANT -20/+80, <sup>HARD TO</sup> EQUALIZE

MAXWELL ULTRACAPS ABOUT \$5 EACH, THAT MAKES \$120 FOR THE PACK, NOT COUNTING CONSIDERABLE PC BOARD COST PLUS ANCILLARY COMPONENTS, MUST ASK MYSELF, DO I REALLY WANT TO RUN BATTERYLESS?


- VEHICLE WAS NEVER INTENDED TO BE PRACTICAL, NEED NOT CONSIDER COST, NOR MANUFACTURABILITY
- WOULD LEARN ABOUT ULTRACAPS IN PROCESS
- WOULD I WANT TO TAKE IT ACROSS DEATH VALLEY?
- ENOUGH FOR DEMO ON STAND
- BATTERY NOT ~~BETTER~~ BETTER THAN CAP ON LONG TRIP - STILL MUST RECHARGE.

29 MAY 2014  
Rodenick.


# SUPERCAP EQUALIZATION CIRCUIT,

NOT WORRIED ABOUT THROWING AWAY POWER - HAVE  
CONSTANT SUPPLY FROM SUN,

~~AM CONCERNED~~

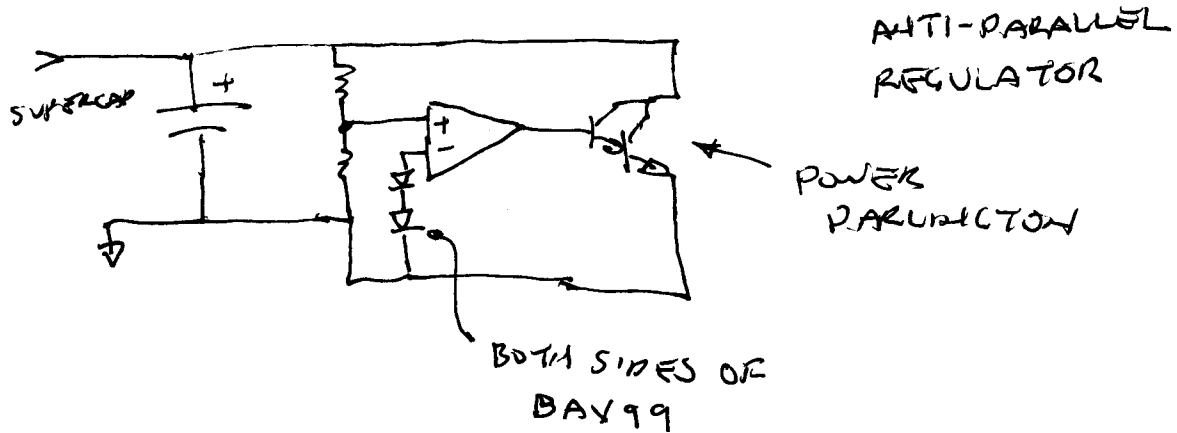

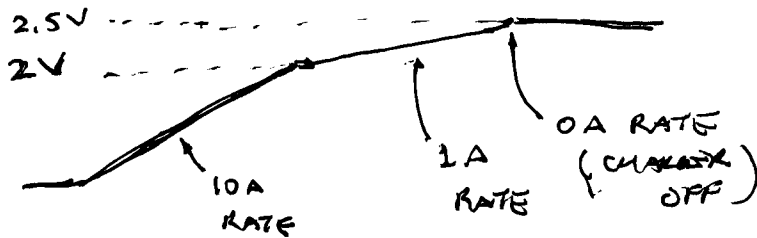STACK OF  
IDEALLY, CHARGE CAPS AT MAX RATE, BUT WHEN  
IT GETS CLOSE TO ~~V~~ VOLTAGE WHERE ANY SHUNT  
COULD ACTIVATE, SLOW CHARGING RATE SO  
WON'T BURN OUT DARLINGTON, WHEN FINAL  
VOLTAGE IS REACHED, TURN OFF CHARGER,




BEST DARLINGTON SEEMS TO BE MJD122G - ~~NO BASE-EMITTER~~  
RESISTOR BUILT IN, <sup>OR YES IT HAS</sup> DPAK FOR SURFACE MOUNT, TYPICAL GAIN = 2500,  
AT BASE CURRENT OF 2mA,  $V_{CE(SAT)} = 1V$ , FOR  $I_C = 2A$

FOR OP AMP, USE MCP6001.  $V_{DD} = 1.8V$ . SOT23-5. DOES NOT COME  
IN DIP, BUT MCP6002 IS DUAL UNIT IN ~~POP~~ PDIP-8, GOOD FOR  
PROTOTYPING.

26 MAY 2014; Roderick.

WANT TO PROTOTYPE CAPACITOR EQUALIZATION BEFORE INVESTING IN 25 x \$5 SUPERCAPACITORS. \$5 SHIPPING FROM MOUSER EVERY TIME, BUT DM SAYS BETTER TO PAY THE \$5 THAN RISK \$125 BUYING WRONG THING.

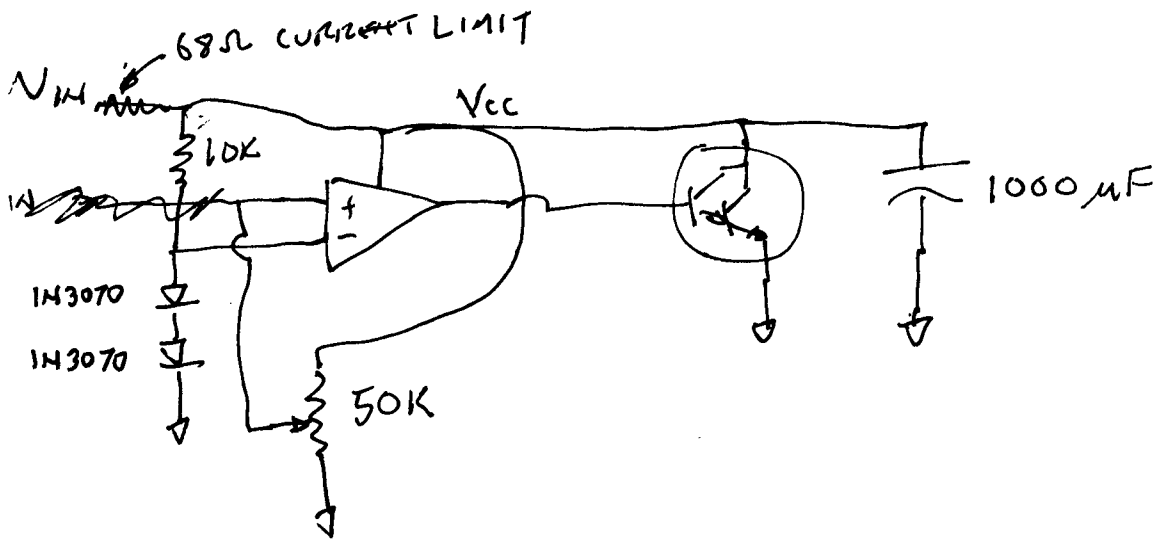BEFORE EVEN ORDERING, WILL PROTO W/ LM358. NO LOW VOLTAGE OP-AMPS AVAILABLE AT RETAIL STORES, SO WILL GO WITH THAT 3V OP-AMP, AND AIM FOR TARGET REGULATION AT 4V.



DIODES ARE NOT VERY CONSTANT VOLTAGE. AT  $V_{in} = 2.0V$ , DIODE DROPS ARE 1.0V. AT  $V_{in} = 2.7V$ , DIODE DROPS ARE 1.06V. @  $V_{in} = 2.5V$ , DROP = 1.04V. GOOD ENOUGH FOR PURPOSE, THOUGH. ONLY MATTERS THAT DIODE IS MORE CONSTANT THAN RESISTIVE DIVIDER.  $V_{in} = 4V$ , DROP = 1.09V. INPUT VOLTAGE CHANGED 100%, DIODE CHANGED 9%. SURE ENOUGH, COMPARATOR OUTPUT GOES TO  $\approx 3V$  AS SOON AS SUPPLY VOLTAGE = 4.0. AT 3.9V, COMPARATOR OUT = 0. NO OUTPUT FROM COMPARATOR EVEN @ SUPPLY = 1.1V. VERY GOOD REGULATOR, ~~IF~~  $V_{CC}$  STAYS AT 4V WHEN INPUT SUPPLY IS 5V.





SUPPLY CAP STACK  
 SUPPOSE ALL CAPS ARE C,  
 BUT ONE CAP IS 1.1 C  
 WORST CASE WOULD BE ALL CAPS  
 0.8 C, AND ONE 1.2 C,  
 BUT I THINK THAT  
 UNLIKELY IN ONE  
 LOT, AND I CAN

CHARACTERIZE.

THAT TURNS OUT 11 EQUALIZERS  
 WHILE ONE CAP IS  
 CHARGING.



LOSS IN B-E  
 RESISTOR OF  
 PARLINGTON  
 FOR EQUALIZER

OPPOSITE CASE, 1 EQUALIZER  
 ON, WANT TO LIMIT CHARGE  
 CURRENT IMMEDIATELY.

$$\frac{0.5V}{8K\Omega} = \frac{1}{16K} = \frac{1}{16} mA$$

ALL CAPS 1.1 C, ONE CAP = C  
~~0.9 C~~ CAP WITH C HAS  
 VOLTAGE OF 2.5V, EQUALIZER ON.  
 OTHER CAPS HAVE  $\frac{2.5}{1.1} \approx 2.27V$   
 BUT 11 OF THEM, SO STACK HAS

~~2.27~~ OUT OF  
 2 MA

EVEN IF 0.8V, STILL

$\frac{1}{10} mA$  OUT OF 2 MA  
 ⇒ NOT SIGNIFICANT

$$\frac{2.5}{1.1} \cdot 11 = 25 \text{ VOLTS. TOTAL VOLTAGE}$$

ACROSS ALL 12 IS  $25 + 2.5 = 27.5V$ , MEANING CHARGER  
 SHOULD LIMIT TO 2A WHEN THAT VOLTAGE IS ACHIEVED.

WORST CASE, 11 CAPS AT 1.2C, ONE CAP AT 0.8C  
 SAME AS 1.5C VS. C.

Map data ©2014 Google

$$\text{STACK OF 11: } \frac{2.5 \cdot 11}{1.5} = \frac{5 \cdot 11}{3} = 18.3V$$

$$18.3 + 2.5 = 20.8V$$

↳ current limit point.


These directions are for planning purposes only. You may find that construction projects, traffic, weather, or other events may cause conditions to differ from the map results, and you should plan your route accordingly. You must obey all signs or notices regarding your route.

31 MAY 2014; Roderick


GOT Mouser parts, will try real equalizer circuit now, MJO 122G is smaller than I expected, it's a DPAK, not DPAK-2.



MJO122G

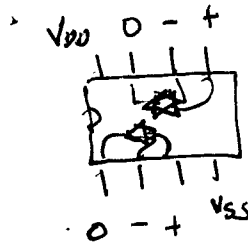

MCP6002  
SAME PINOUT AS  
LM358

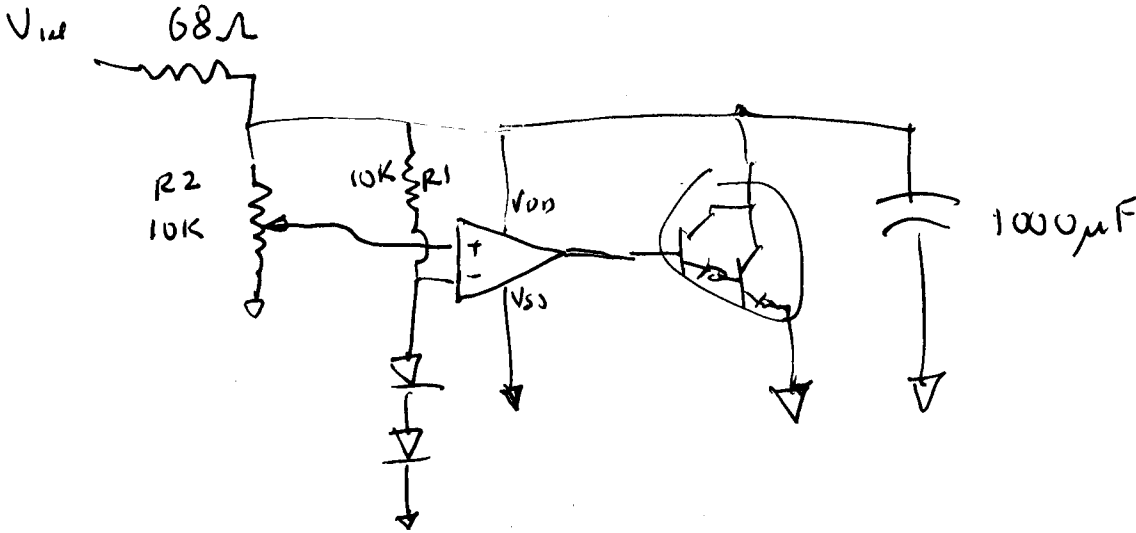

SET POTENTIOMETER R2 FOR 2.5V OUTPUT VOLTAGE, SEEMS STABLE ACROSS RANGE OF 2.5V - 6V =  $V_{in}$

TRY CHANGE R1 TO 100K, NOW OUTPUT IS 1.94V.

RESET R2 FOR 2.5V OUT, REGULATION GOOD OVER 2.5V - 6.6V RANGE.

⇒ SHOULD TEST LATER HOW DIODE  $V_f$  CHANGES

WITH TEMPERATURE.

WARM ROOM, SEEING 2.39V NOW, WILL CHECK AGAIN

WHEN IT GETS COLD.

COOL MORNING - 2.53V


SHOULD SET CIRCUIT FOR 2.7V AT COLDEST POSSIBLE TEMPERATURE. WHEN HOT, CAPS RATED FOR LOWER VOLTAGE.

ANYWAY,


04 JUN 14 TRIED EQUALIZER w/ REAL 50F CAPACITOR, SEEMS TO WORK.

03 JUN 2014, Radenk.
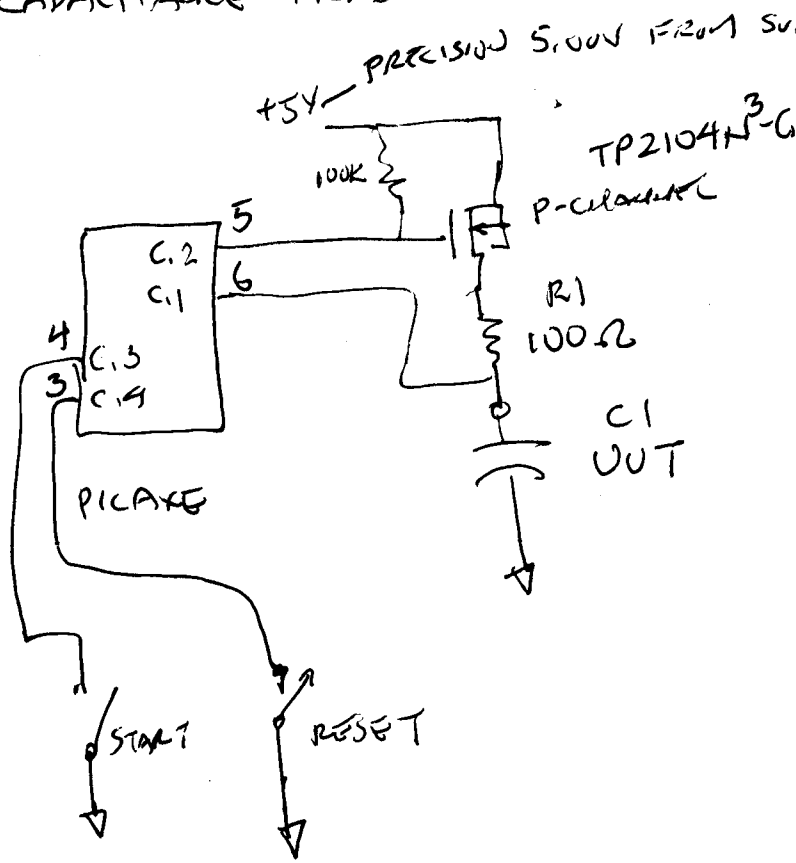
# CAPACITANCE MEASUREMENT OF SOF CAPACITORS,



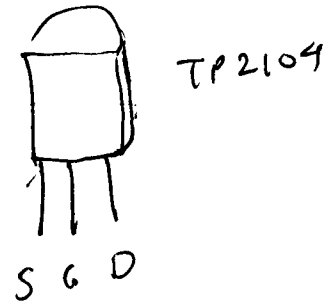PROGRAM SAMPLED  
ONCE PER SECOND  
UNTIL



BEFORE USING REAL SUPERCAP, TEST PROGRAM  
AND CIRCUIT USING  $R1 = 10k\Omega$ ,  $C1 = 1000\mu F$   
TIME CONSTANT SHOULD BE 10 SECONDS,  $\rightarrow$  LOOKS OK.

TRYING CAPACITOR 1,  $100\Omega = R1$   $V_{DD} = 5.0V$

TIME = 4461 SEC

$$V = 5.0 (1 - e^{-t/R_1C}) = 2.5$$

$$0.5 = 1 - e^{-t/R_1C}$$

$$e^{-t/R_1C} = 0.5$$

$$-t/R_1C = \ln(0.5) \quad \frac{t}{R_1C} = \ln(2)$$

$$C = \frac{t}{R \ln(2)} = \frac{t}{100 \cdot 0.693} = \frac{t}{69.3} \quad \text{FIRST CAP} = \frac{4461}{69.3} = 64.4F$$

IF  $R_{DS(on)}$  OF MOSFET =  $6\Omega$ , THEN CAP IS REALLY  $\frac{100}{106} \cdot 64.4 = 60.7F$

SECOND CAPACITOR  $t = 4373$  SEC,  $\Rightarrow C = 63.1F$

CAPACITORS ARE WITHIN 2% OF EACH OTHER, ENCOURAGING,  
OR 59.5F IF  $106\Omega$  ASSUMED.