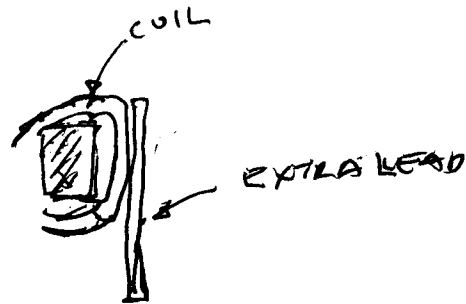


WOUND CUSTOM ~~FOR~~ TOROID



LEAD 1 IS DIRECT WIRE
LEADS 2-13 HAVE EXTRA WIRE
SOLDERED ON TO EDGE OF
COIL



INDUCTANCE MEASURED LEADS (INCLUDING JIG)

1-2	4.0 μ H	1-3	8.4 μ H
2-3	3.9 μ H	1-4	15.6
3-4	3.9	1-5	25.8
4-5	3.9	1-6	38.9
5-6	4.0	1-7	55.0
6-7	4.0	1-8	74.3
7-8	4.0	1-9	96.5
8-9	4.0	1-10	122.5
9-10	4.0	1-11	152.7
10-11	4.0	1-12	188.0 μ H
11-12	4.0	1-13	0.234 mH
12-13	4.0		

02 FEB 2015;
Roderick.

PREVIOUS EQUATIONS

$V =$ INPUT SUPPLY

$L =$ INDUCTANCE OF MAIN TOROID

$t =$ CHARGING TIME, HALF OF PERIOD

$P =$ ~~OUTPUT~~ ^{INPUT} POWER (OUTPUT ASSUMED SIMILAR)

~~$V_F =$~~

$$t = \frac{4PL}{V^2}$$

SAG IN INPUT CAP VOLTAGE (DISREGARDING PANEL)

$C =$ INPUT CAPACITANCE

$V_F =$ ~~FINAL~~ CAPACITOR VOLTAGE AFTER CHARGING INDUCTOR

ALSO MAKE ASSUMPTION THAT SAG IS SMALL, ELSE EQUATION INVALID.

$$V_F = \sqrt{V^2 - 16 \frac{P^2 L}{C V^2}}$$

$$C = \frac{16 P^2 L (V^2 - V_F^2)}{V^2 (V^2 - V_F^2)} = \frac{4PL}{(V^2 - V_F^2)}$$


SUPPOSE I ACTUALLY WANT TO USE ENTIRE 12 WINDINGS OF TOROID @ $234 \mu H$, ASSUME $P = 200W$ WORST CASE, $V = 24$ VOLTS

$$t = \frac{4 \cdot 200 \cdot 234 \cdot 10^{-6}}{24^2} = 325 \times 10^{-6} \quad 325 \mu S$$

FOR 1 VOLT DROOP

$$C = \frac{16 \cdot 200^2 \cdot 234 \cdot 10^{-6} (24^2 - 23^2)}{24^2} = \frac{4 \cdot 200 \cdot 325 \times 10^{-6}}{(576 - 529)} = \frac{260000}{47} \times 10^{-6} \approx 5531 \mu F$$

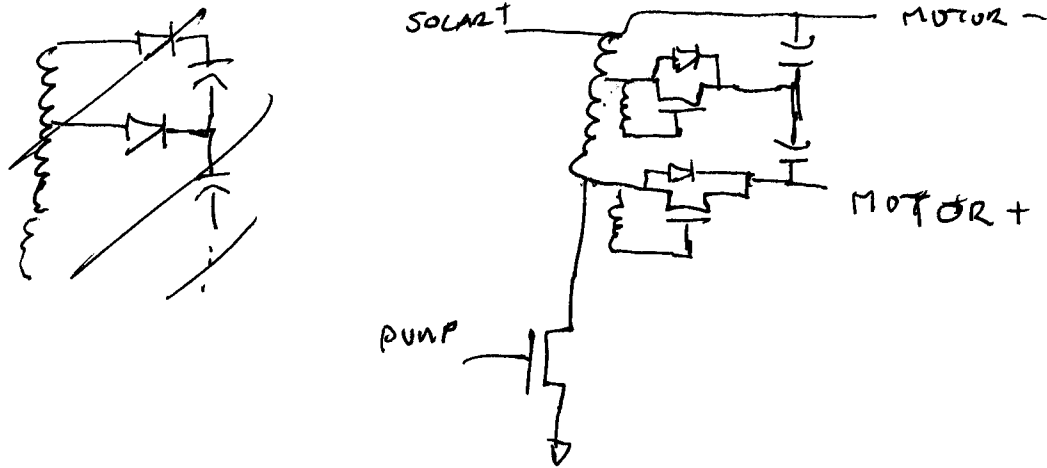PROBLEM WITH USING SINGLE INDUCTOR TO CHARGE CAPACITOR STACK?



CAN V_{GS} OF SYNC RECTIFIERS EVER GO OUT OF SAFE ZONE?

WHEN PUMPING, V_{DS} MAY BE $40 + 30 = 70V$ FOR BOTTOMMOST RECTIFIER. BUT V_{GS} SHOULD BE BASED ONLY ON TURNS RATIO BETWEEN WHOLE INDUCTOR AND GATE WINDING.

WOULD LIKE V_{GS} TO BE LARGE AS POSSIBLE FOR QUICK TRANSITIONS. BUT WAIT, IS THAT TRUE? IT'S TRUE FOR RESISTIVE DRIVE. WITH TRANSFORMER, THE WINDING WILL TAKE ALL THE CURRENT IT CAN OVERCOMING THE MILLER CAPACITANCE OF THE GATE BEFORE IT LETS ANY OF THE MAIN WINDINGS RISE HIGHER. HIGHER V_{GS} DOES MEAN SLIGHTLY LOWER $R_{ps}(on)$ THOUGH.

BUT CANNOT VIOLATE $\pm 20V$ V_{GS} RATING OF ALL THE COMMON MOSFETS I'M CONSIDERING.

IF MAIN INDUCTOR IS 12 TURNS, AND $-40V$ MAX PURING PUMP, 6 TURNS FOR GATE WINDING WOULD BE $-20V$.

WILL MAKE TABLE ON NEXT PAGE.

GATE WINDING VOLTAGES - ASSUME DRIVE 12T OF INDUCTOR
 PUMP VOLTAGE = 24V CAPACITOR STACK VOLTAGE = 30V

GATE TURNS	PUMP V_{GS}	CHARGE V_{GS}	
6	-20	15	; RIGHT ON THE EDGE
5	-16.7	12.5	← USE THIS, HAS MARGIN
4	-13.3	10	
3	-10	7.5	
2	-6.7	5	; TOO LOW

IF DECIDE TO DRIVE 8T OF MAIN INDUCTOR ONLY

GATE TURNS		
6	-30	22.5
5	-25	18.75
4	-20	15
3	-15	11.25
2	-10	7.5

GIVE UP ON DRIVING INDUCTOR AT MIDDLE TAP. ONLY ADVANTAGE WOULD BE HIGHER OPERATING FREQ. DRIVING WHOLE INDUCTOR WILL DISTRIBUTE MAGNETIC FIELD AROUND TOROID BETTER. BUT WHAT IF ACTUAL SOLAR INPUT IS 24 VOLTS?


CHARGE $V_{GS} = 24 \cdot 5 / 12 = 10V$ THAT'S OKAY

Blue Shield of California

IF I USE 5 TURNS ON GATE WINDING, GATE VOLTAGE = $\frac{5}{12}$ OF THE VOLTAGE ACROSS THE WHOLE INDUCTOR. IF THE SOLAR INPUT IS 12 VOLTS, THE SYNCHRONOUS RECTIFIERS WOULD BE DRIVEN BY JUST 5 VOLTS = V_{GS} . BARELY BETTER THAN JUST PLAIN ~~RECTIF~~ PASSIVE RECTIFIERS. COULD RUN WITH 12 VOLT INPUT JUST TO SHOW IT WORKS, BUT WOULDN'T BE AS EFFICIENT. BIG SOLAR PANELS AREN'T 12 VOLTS ANY MORE, ANYWAY. DROP 12 VOLT INPUT AS A REQUIREMENT. COULD REWORK BOARD & DRIVE INDUCTOR AT MIDDLE TAP FOR 12 VOLTS. ~~NOT TRUE~~ - $V_{GS} = \frac{5}{12}$ OF OUTPUT VOLTAGE, STILL GOOD.

SOFTWARE SHOULD DETECT INPUT VOLTAGE OUT-OF-RANGE AT INIT, AND FLASH ERROR LIGHT, RS-232 CONNECTION REQUIRED FOR DETAIL.

EXPERIMENT:

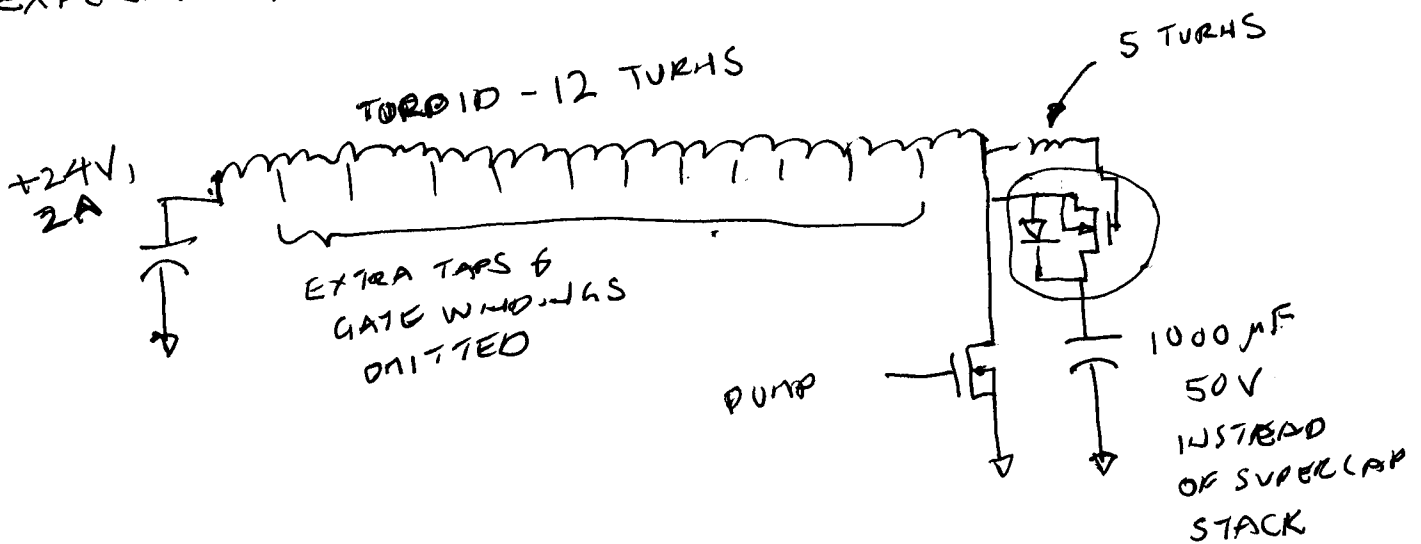

06 FEB 2015;
Roderick.

WILL RUN EXPERIMENT ON PREVIOUS PAGE. HAVE A POWER BRICK CAPABLE OF 24V, 2A. HAD SLA BATTERIES BEFORE, BUT THEY WENT BAD. SO WILL ONLY ~~CHARGE~~ PUMP INDUCTOR TO 2A FOR THIS TEST.

$$dI = \frac{V}{L} dt$$


$$2 = \frac{24}{234 \times 10^{-6}} dt$$

$$2 = \frac{24}{24 \times 10^{-5}} dt$$


$$dt = 20 \times 10^{-6} = 20 \mu\text{S}.$$

MUST CHANGE PICAXE PROGRAM TO DELIVER SINGLE PULSE OF THIS ~~MAGN~~ DURATION.

10 FEB 2015; Roderick

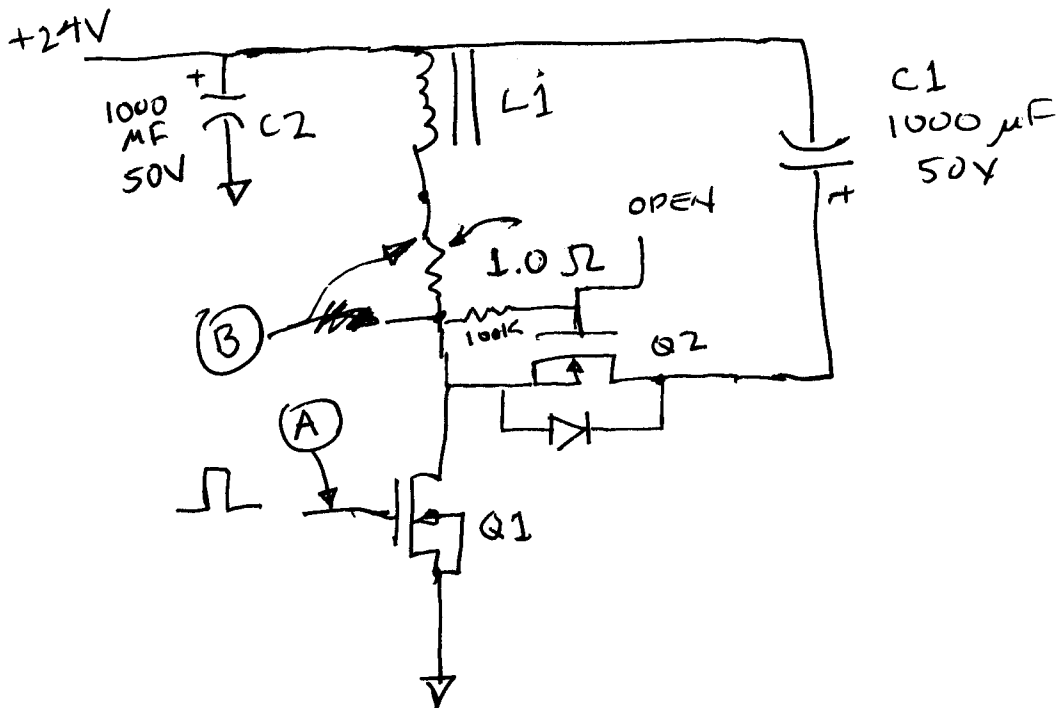

HOOKED UP EXPERIMENT, PUT 20MS, 12V PULSE IN AT (A). VOLTAGE ON C1 ONLY RISES BY 0.01 TO 0.02V PER PULSE. SHOULD BE MUCH MORE, LIKE 1 VOLT IF 100% EFFICIENT. I WAS THINKING THAT INDUCTOR MIGHT BE LARGER THAN MEASURED, OR SOMETHING IN THE DRIVE PATH IS OTHERWISE NOT ALLOWING THE FULL 2 AMPS TO BUILD UP. CAN'T BE DC RESISTANCE OF L1 - THAT JUST ABOUT 1 METER OF #12 COPPER. MAYBE C2 WAS NOT SUPPLYING ENOUGH CURRENT, OR 24V SUPPLY JUST TOO WEAK? COULDN'T BE Q1 NOT TURNING ON, COULD IT? NEEDED TO PROBE CIRCUIT - PUT SCOPE AT POINTS (A) AND (B)

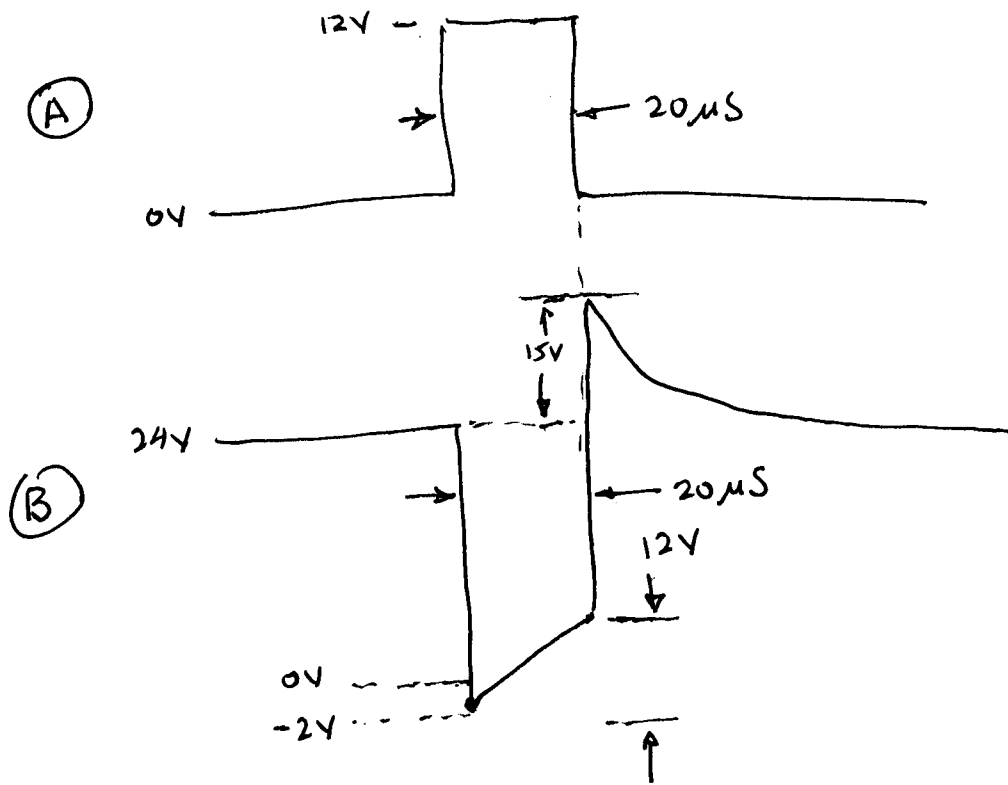

3 THINGS STRANGE:


- 1) LOOK AT SLOPE OF VOLTAGE ACROSS 1Ω RESISTOR, 12V RISE IN 20 μS, IF DRIVEN BY AN AVERAGE VOLTAGE OF 18V, THAT SUGGESTS L_1 IS REALLY 30 μH, NOT 240 μH.
- 2) UNDERSHOOT BELOW GROUND, ON A PREVIOUS TRACE WITHOUT THE 1Ω RESISTOR, THE BOTTOM OF THE (B) TRACE WAS FLAT, AT -5V OR SO, FOR THE WHOLE 20 μS, NOT JUST AN UNDERSHOOT.
- 3) WHEN Q1 TURNS OFF, I EXPECT (B) TO JUMP, BUT THEN EITHER STAY FLAT OR SLOWLY RISE, AS THE CAPACITOR C_1 CHARGES, EXPONENTIAL DELAY IS NOT EXPECTED,

REGARDING QUESTIONS FROM IOFEBIS (ANOMALIES):

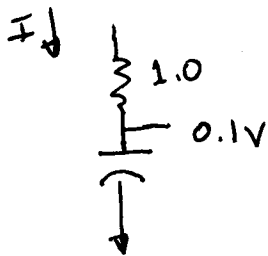1) SUBSTITUTED 0.05Ω INSTEAD OF 1.0Ω AS SENSE RESISTOR. STILL SEE RAPID JUMP IN CURRENT, SUGGESTING 24 A AFTER 20 μ S, (1.2 V ACROSS 0.05Ω), THAT WOULD MAKE INDUCTOR $\frac{24V}{24A} \cdot 20\mu S = 20 \mu H$.

OKAY, SO MAYBE THE DM4070 METER IS NOT A GOOD MEASURE FOR INDUCTANCE AT HIGH CURRENTS? IF L_1 IS REALLY 20 OR 50 μH , ALL THE BETTER FOR DESIGN - WON'T HAVE TO GO TO LOWER FREQUENCIES, AND CAN USE SMALLER INPUT CAPACITORS.

ALSO NOTED THAT WITH 0.05Ω , OUTPUT VOLTAGE JUMPS 0.25, MAYBE 0.35 V AT A TIME. MAKES SENSE.



FOR SHORT PULSE OF 12 AMPS, 12 V DEVELOPS ACROSS R. $P = I R$, SO ONLY 4% OF POWER GOES INTO CAP (DISREGARDING THAT VOLTAGE RISES).

IF $R = 0.05 \Omega$, VOLTAGE IS $12/20 = 0.6 V$ ~~AND~~ MEANS $\sim 15\%$ OF POWER GOES TO CAP

DISREGARDS DIODE DROP OF ~~NON-SYNCHRONOUS~~ PASSIVE RECTIFIER, WHICH IS SIGNIFICANT.

THIS TELLS ME THAT OUTPUT RESISTANCE MATTERS A LOT, AND THAT THERE IS AN EFFICIENCY LIMIT AT LOW VOLTAGES, ~~LIKE 6~~ HIGH CURRENTS, ~~EVERIF~~ A CONCERN WHEN INDIVIDUAL SUPERCAPS ARE CHARGED TO JUST 2.5V. MAKES SYNCHRONOUS RECTIFICATION A MUST.

MORE EXPERIMENTS:


CHARACTERIZE VOLTAGE VS INDIVIDUAL PULSES FOR 0.05Ω
RESISTOR SETUP, THEN AGAIN WITH RESISTOR REMOVED (SHORTED).

PULSE	VOLTAGE	
0	0.03	; STARTING VOLTAGE
1	0.05	
2	0.07	

VP TO 24V OR 30V IF POSSIBLE,

MAYBE SHOULD USE A/D OF PICAXE, AND PUT OUT ONE
PULSE PER SECOND, THEN REPORT OVER RS-232


STOP AFTER READING FINAL VOLTAGE

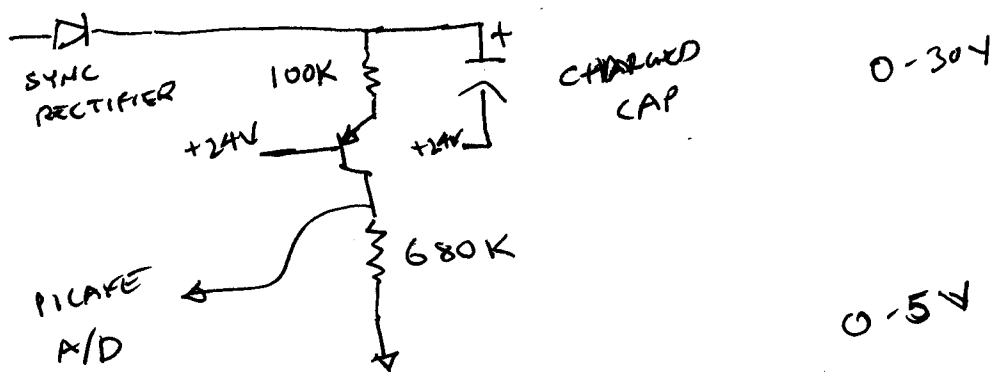


ALSO TRY WITH SYNCHRONOUS RECTIFIER ENABLED.

ALSO TRY CHARGING JUST ONE SUPERCAP - MAY NEED
TO JUST USE ONE PULSE PER SECOND (OR 100), AND
NOTE RESULTS MANUALLY ON VOLTMETER. BASE-EMITTER
DROP ON SENSE CIRCUIT COULD DISTURB ACCURACY AT
LOW VOLTAGES.

DECIDED TO DO AUTOMATIC MEASUREMENT.

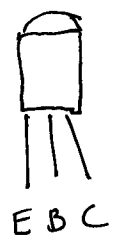

2N3906

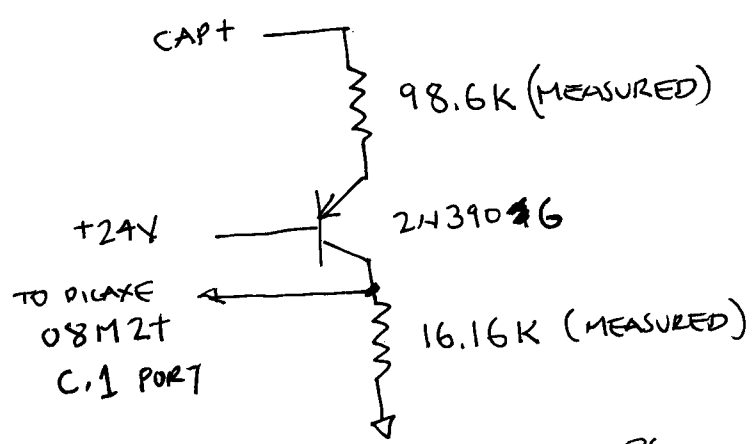

FULL SCALE VOLTAGE ON PICAXE = 5.0V = ~~1023~~ ^{ADC} 1023 UNITS

$$V_p = \frac{C_p \cdot V_c}{98.6} \cdot \text{CAP VOLTAGE}$$

(V_p)

$$V_p = \frac{C_p \cdot 5}{1023}$$

COUNT

$$V_c = V_p \frac{98.6}{16.16} \cdot \frac{5}{1023}$$

$$V_c = \text{CAP VOLTAGE} \cdot \frac{98.6}{16.16} \cdot \frac{5}{1023}$$

↑ PICAXE COUNT

CONSTANT FOR SPREADSHEET.

WROTE PROGRAM TO PUT OUT ONE PULSE PER SECOND. AT THAT RATE, THE ~~PI~~ CHARGING LEVELS OUT AT ABOUT 10.6 VOLTS, 100K IS TOO MUCH OF A LOAD, COULD UP THE FREQUENCY OF CHARGING, BUT THINK I SHOULD DETERMINE WHETHER CAN USE 1 MΩ IN TOP RESISTOR AND 162K IN BOTTOM w/ PICAXE. WITH VOLTMETER CONNECTED, CAP CHARGES MUCH HIGHER. DON'T KNOW IMPEDANCE OF METER, BUT IF 50KΩ/VOLT ON 20V SETTING, THAT'S 1 MΩ

13 FEB 15; Roderick.

CHANGED RESISTORS TO 1M (1005K MEASURED) AND
150K (154.2K MEASURED). NOW CAN ACHIEVE A COUNT OF
951 ~ 954, WHICH TRANSLATES TO 30.4V. BUT STILL,
IT'S LEVELING OFF WITHOUT REACHING COUNT OF 1000 ON A/D.
SO SUGGESTING THAT THE TEST SIG IS STILL DISTURBING THE
READING SIGNIFICANTLY. NOTE: GOOD THING I DIDN'T TRY TO
MEASURE MANUALLY WITH A VOLTMETER, I REALIZE NOW THAT
I WOULD HAVE HAD TO WRITE DOWN HUNDREDS OF FIGURES.
ONE MORE THING TO TRY - PUT A CAPACITOR ACROSS LOWER
RESISTOR. IF THAT INCREASES THE READING, CONCLUSION WOULD
BE THAT A/D ~~IMPEDANCE~~ IS DRAWING TOO MUCH CURRENT
DURING SAMPLING. IN FACT, MIGHT AS WELL ALWAYS HAVE A
SMALL CAP IN FINAL DESIGN. ALSO WANT A PNP TRANSISTOR
IN FINAL DESIGN W/ HIGH GAIN @ LOW CURRENT.

CAPACITOR DETERMINATION: GO FOR TIME CONSTANT CONSIDERABLY
SHORTER THAN PULSE REPETITION RATE.

SAY, $1 \text{ms} = 10^{-3} \text{ SEC} = 5 \text{ TIME CONSTANTS}$

$\tau = 200 \times 10^{-6} = RC$ R IS 150K PARALLEL 1 MEG.


$$C = \frac{200}{150} \times 10^{-9} = 1300 \text{ pF}$$

PUT IN 2700 pF - ONLY PULSING AT 1 SEC INTERVALS NOW,
NOW LEVELING OUT AT 956-959 COUNT, MINIMAL DIFFERENCE.

13 FEB 15; Roderick.

CHANGED RESISTORS AGAIN, TOP = 3.3M, BOTTOM = 470K,
NOW COUNT IS GOING ALL THE WAY TO 1007, WHERE THE
PROGRAM AUTOMATICALLY STOPS PULSING. 862 ~~SEE~~ PULSES TO
GET THERE.

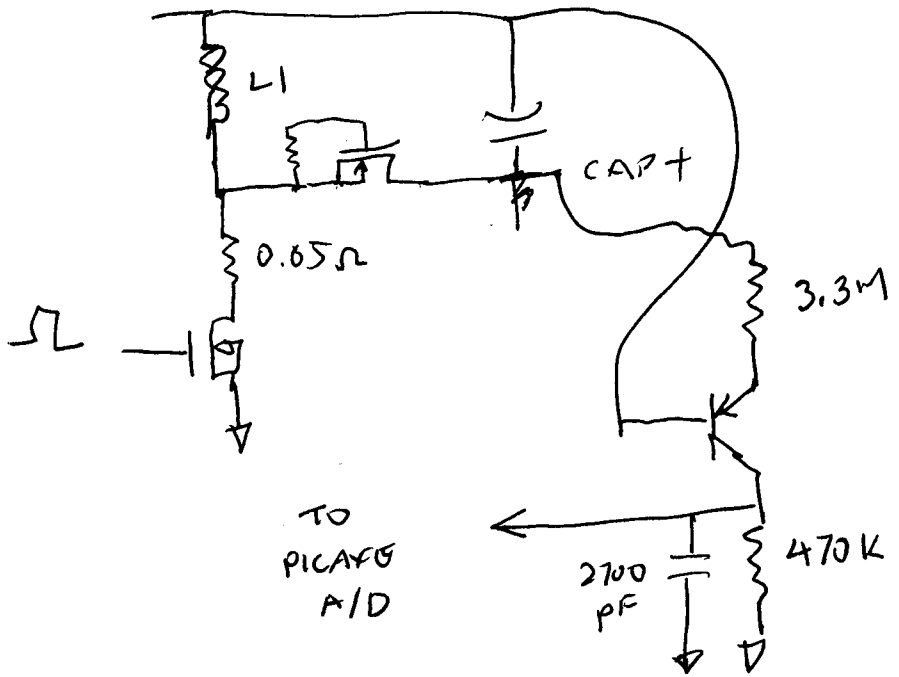REMOVED 0.05Ω RESISTOR, SOLDERING DIRECTLY INSTEAD,
TOOK ONLY 676 ^{PULSES} ~~COUNTS~~ TO GET TO 1007



LOOKS LIKE ALMOST ~~25%~~ 27.5% OF POWER LOST
TO 50mΩ RESISTOR

$$\frac{862 - 676}{676} = \frac{186}{676} = .275$$

CRITICAL TO KEEP RESISTANCES LOW IN ACTUAL DESIGN,
THIS EXPERIMENT ALSO VALIDATES THE VOLTAGE
SENSING ARRANGEMENT.