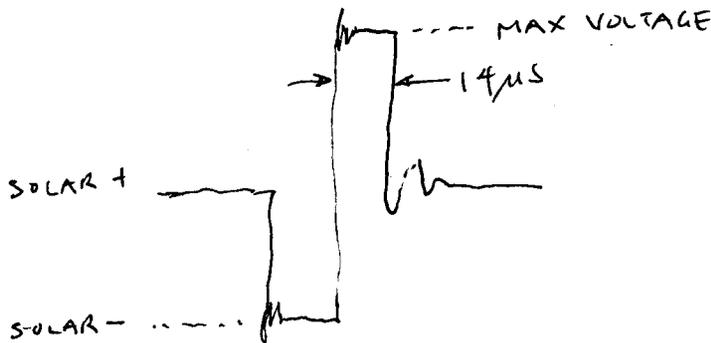


09 MAR 2015;  
Roderick.

PREPARING TO WIND T300A-26 TOROID. WRAPPED #26 WIRE 12T AROUND IT. LENGTH WAS 43" - WILL GO 48" WITH #10, AND TRIM. PUT A PAPER BAND AROUND TOROID. OUTER CIRCUMFERENCE SEEMS TO BE 243-244 mm. ~~PRINTER~~ TRIED PRINTING A BAND 244 mm ~~LONG~~. LONG. EITHER MY RULER WAS OFF, OR THE PRINTER WAS. WILL TRY AGAIN WITH 242 mm. NO, 243 SEEMS RIGHT, NOW. AS HARD TO WIND AS PREVIOUS TOROID. MADE COMPONENT IN DESIGNSPARK WROTE SMALL C PROGRAM TO CALCULATE COORDINATES OF 13 EQUALLY SPACED HOLES ON 243 mm CIRCLE.

19 MAR 2015. TRIED IT IN CIRCUIT - WORKS WELL. POSSIBLY DUE TO LOWER INDUCTANCE, CHARGE TIME IS FASTER THAN HURRICANE INDUCTOR. ALSO, ON SCOPE OBSERVED MINIMUM PULSE WIDTH OF CHARGING IS 14  $\mu$ S, NOT 12  $\mu$ S AS BEFORE.



RINGING AFTER CHARGE ENDS IS SLOW - 210 KHZ. DON'T WANT TO LOSE ENERGY SHUDDING IT. HOWEVER, WITH SHUDDING HIGHER FREQ RIBBLG AT START OF PUMP + CHARGE - IT THREATENS GATE OF MOSFET.


WILL HOOK UP GATE OF SYNCHRONOUS RECTIFIER. PULSE LIMIT IS TUNED FOR 12  $\mu$ S PULSE RIGHT NOW, BUT WILL JUST LEAVE IT. TOO SHORT DOES NO HARM FUNCTIONALLY, JUST IMPACTS EFFICIENCY. OUTPUT STAYS AT BASICALLY  $\phi$ . FOUND NEW TOROID WIRED BACKWARDS. MADE NO DIFFERENCE FOR NON-SYNC CASE. FIXED.

MISTAKE #2, GATE WINDING WOULD IN WRONG DIRECTION. CORRECTED.  
W/O SYNC RECTIFY, COUNT TO 1007 = 271  
WITH " " " " " = 264 HELPS A LITTLE.  
CAN TUNE LATER





21 MAR 2015;  
Roderick.

TUNED PULSE LIMITER R TO 1.5K $\Omega$

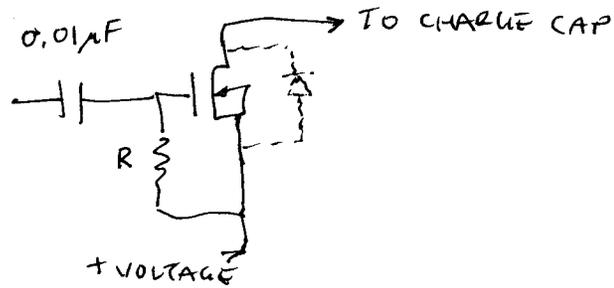

COUNT TAKES 264 20 $\mu$ S PULSES TO CHARGE CAP TO MAX VOLTAGE.  
NO IMPROVEMENT. NEEDED SEVERAL TRIALS TO MAGNETIZE CORE  
UNTIL COUNT WAS STABLE. TRY AGAIN WITH R = 2.51K  
TOOK 313. SEEMED TO BE STRUGGLING AT NEAR TOP. TRY AGAIN.  
SCOPE SHOWS MOSFET NOT TURNING OFF IN TIME. TRY 2K. STILL  
TROUBLE AT OUTPUT VOLT = 25 OR SO. TRY 1.7K - RING @ 930<sup>COUNT</sup>  
TRY 1.51K - RING @ 954. TRY 1.3K - OK. COMPLETES @ 265.  
TRY 1.2K - 264 TRY 1.0K - 261 TRY 700 $\Omega$  - 264

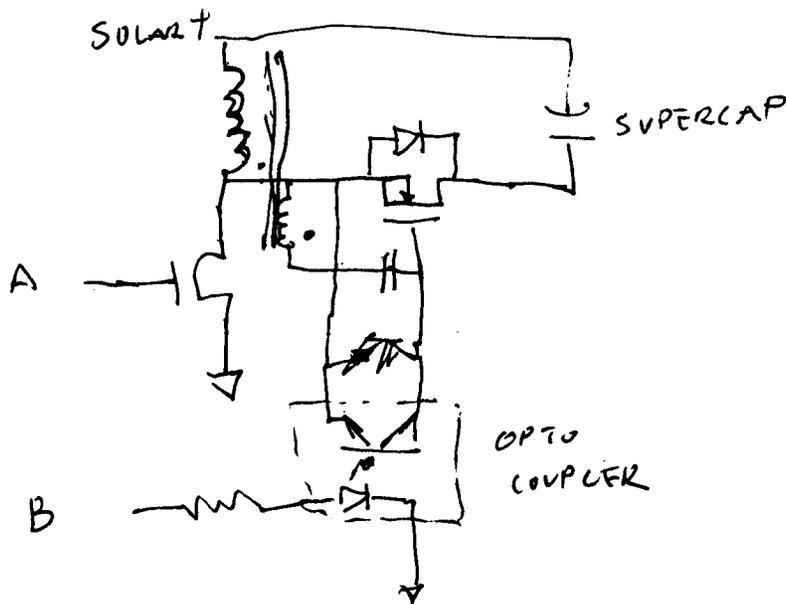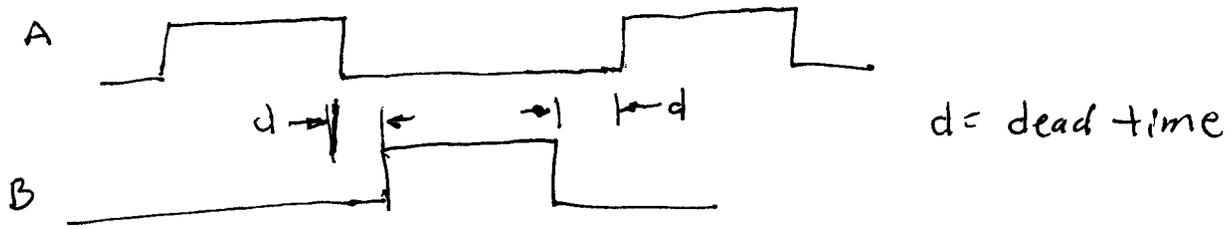ALTERNATE WAY OF TURNING OFF SYNCHRONOUS RECTIFIER IF  
SNUBBER FAILS



A AND B USING HALF BRIDGE OF HWPWM OF 14M2+



01 MAY 2015  
Rudrick,

GOING TO TRY SNUBBER TO ADDRESS RINGING ON SYNC RECTIFIER.  
NOT GETTING MUCH BENEFIT, W/ PRESET PULSE-LIMITING SCHEME,  
ALTHOUGH GETTING SOME.

RE-WOUND GATE WINDING OF TOROID TO 6 TURNS.

PICAXE 08M2T NOT RESPONDING. CAN'T EVEN CHECK FIRMWARE REV  
W/ AXEPAD OPTION MENU. TRIED READING MODPROBE, NO HELP.  
CHANGED PART, THEN COULD READ FIRMWARE. NOTICED ORIGINAL  
PART SEEMED A LITTLE LOOSE. PUTTING ORIGINAL BACK IN  
BREADBOARD. NUPE, BURNED OUT. CAN'T TELL WHAT DID IT. WAS  
WORKING FINE A FEW DAYS AGO. MAYBE JUST REACHED END OF  
PROGRAMMABILITY? WILL NEED TO BRING SPARE PICAXES IF GO  
IN FIELD. — POSSIBLE THAT RINGING TRANSIENT GOT  
THROUGH & BURNED OUT A/D.

03MAY15. AT ABOUT COUNT 270, RINGING ISSUE STARTS AGAIN.

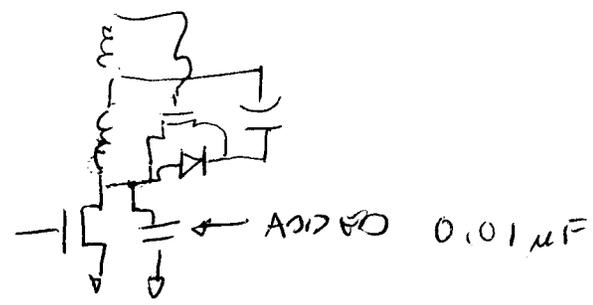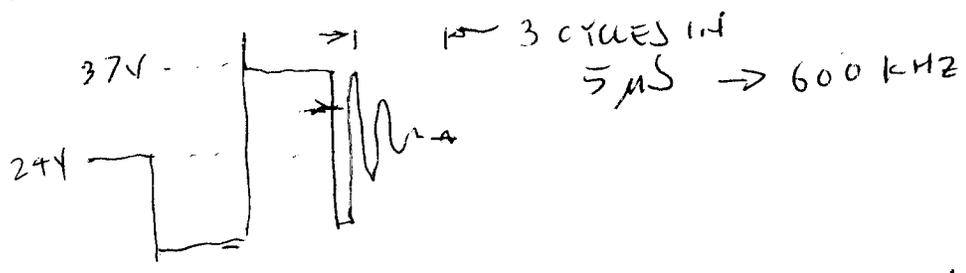

ADDED 0.01 μF, FREQ OF  
RINGING NOW 10 μS / 3 CYCLES  
→ 300 KHZ  
VOLTAGE ONLY GOES TO 250 A/D  
COUNTS INSTEAD OF 280 STEADY STATE.

All investing is subject to risk, including the possible loss of the money you invest.  
There are important factors to consider when rolling over assets to an IRA or leaving assets in an employer retirement plan account. These factors include, but are not limited to, investment options in each type of account, fees and expenses, available services, potential withdrawal penalties, protection from creditors and legal judgments, required minimum distributions, and tax consequences of rolling over employer stock to an IRA.  
Advice services are provided by Vanguard Advisers, Inc., a registered investment advisor.


$$\omega = 2\pi f = \frac{1}{\sqrt{LC_0}} = 600 \text{ KHz} \cdot 2\pi$$

$$\frac{1}{\sqrt{L(C_0 + C_1)}} = 300 \text{ KHz} \cdot 2\pi$$

$$C_1 = 0.01 \mu\text{F} = 10,000 \text{ pF}$$

$$C_0 = 3300 \text{ pF, APPROX.}$$
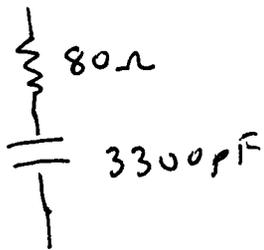
$$Z_{C_0} = \frac{1}{\omega C_0} = \frac{1}{2\pi f C_0} = \frac{1}{2\pi \cdot \frac{6 \times 10^5}{2} \cdot \frac{.01 \times 10^{-6}}{3}}$$
$$= \frac{1}{4\pi \cdot 10^{-3}} = 80 \Omega$$



IDEALLY GOES ACROSS SYNC RECTIFIER  
DRAIN - SOURCE.  
BUT DOES NOT CURE ISSUE OF SYNC  
RECTIFIER NOT TURNING OFF.