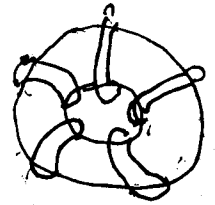


24 APR 13

Roderick


28 $\phi$  INDUCTOR FROM HALTED IS MARKED 10 $\mu$ H  
10A, SPECS SAY 58% OF INITIAL PERMEABILITY  
AT 10A. NEED MORE CROSS SECTION  
ON THE TORROID TO AVOID SATURATION.  
MAY HAVE TO WIND MY OWN  $\frac{1}{2}$  ON  
A BIGGER CORE. BAD THING  
ABOUT SURPLUS CORES, DON'T KNOW WHAT  
KIND OF FERRITE. COULD BE  $\mu=20$ ,  
COULD BE  $\mu=5 \times 10^6$ . NEED TO MEASURE  
INDUCTANCE, BUT DON'T HAVE METER.  
COULD BUILD ONE?



IT'S ABOUT  
THIS SIZE

24 APR 13  
Rodersck.

# MEASURE INDUCTANCE AT WORKING CURRENT

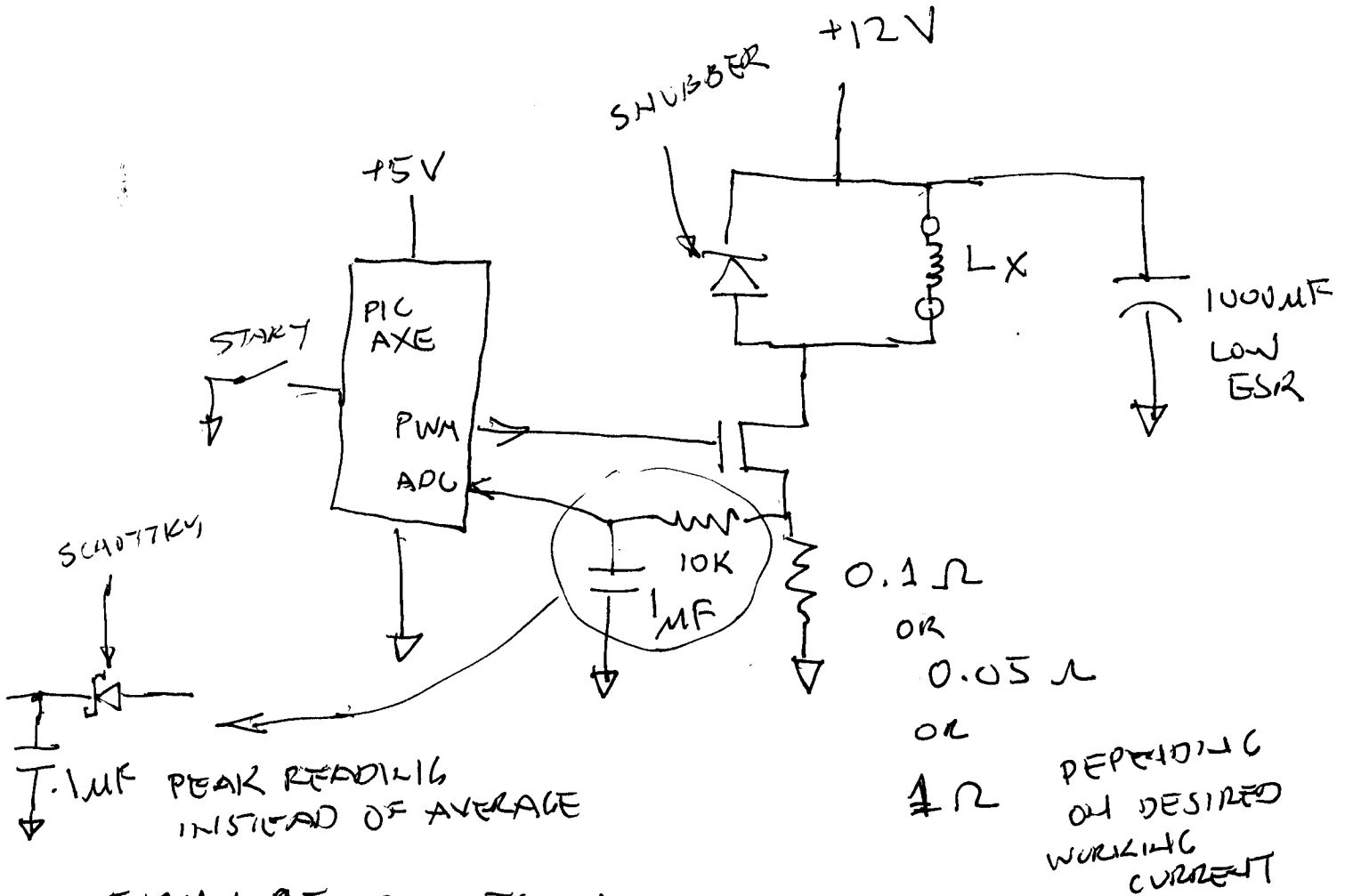

FIRMWARE STARTS AT HIGH FREQ. ON PWM

SWEEPS DOWNWARD UNTIL

CERTAIN VOLTAGE ACHIEVED ON  
ADC. OR ELSE, PEAK READING, LOOK FOR ANY VOLTAGE.  
MUST INITIALIZE ADC OUT


TO 0 FIRST.

# INDUCTANCE MEASURE

24 APR 13

Roderick.


PICAXE COULD DRIVE MULTIPLEXED 7 SEG. UFO DISPLAY HP 5-DIGIT DISPLAY?

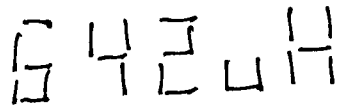
 MICRO


 MILLI


 HENRY

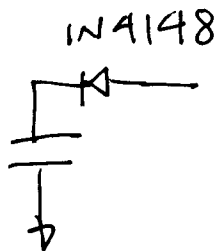FOR PROTO, JUST USE SERIAL PORT TO REPORT



SUPPOSE 1 AMP PEAK AVAILABLE.

1  $\mu$ F

$$i = C \frac{dv}{dt}$$

$$i dt = C dv$$

$$1 dt = 1 \mu F \cdot 5 \text{ volt}$$

$$dt = .5 \times 10^{-6}$$

1 PULSE SHOULD BE ENOUGH

SEC

TO CHARGE CAPACITOR, EVEN AT SHORTEST PULSE.

25 APR 13. NO, PEAK DETECTING INTRODUCES PROBLEMS - DIODE DROP FORCES SOMEWHAT HIGH VOLTAGE (300 mV EVEN IF SCOTTKEY USED), IF USE AVERAGING INTEGRATOR



WILL GET ONLY 1/4


THE VOLTAGE w/ 50%

DUTY CYCLE, BUT COULD

MEASURE RIGHT DOWN TO 1 mV


LOWER  $V_s$  = MORE ACCURATE, EXCEPT FOR NOISE.

INDUCTANCE MEASURE -

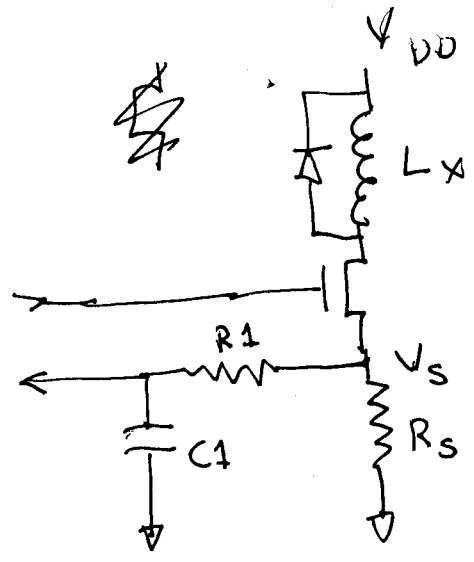

IF USE AVERAGING DETECTOR, NEED TO RUN REPETITIVE WAVEFORM, AND R1C1 MUST HAVE LONG TIME CONSTANT COMPARED TO FREQUENCY.

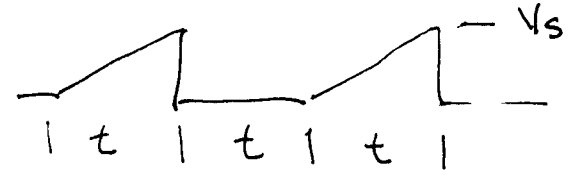SUPPOSE  $V_s = 1V \rightarrow 0V$  SQUARE WAVE.




DURING DISCHARGE, DON'T WANT TO LOSE MORE THAN 1 BIT OF ADC VALUE.  $V_s = 1$  VOLT IS WORST CASE, MIGHT GO WITH 0.1 VOLT.

SUPPOSE  $V_{DD} = 12V$      $L = 8\mu H$      $V = L di/dt$

$$dt = \frac{L}{V} di = \frac{8 \times 10^{-6}}{12} \cdot 40$$

$$dt = \frac{320}{12} \times 10^{-6} = \frac{80}{3} \times 10^{-6} = 27 \mu s$$

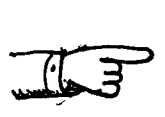
YES, 40 AMPS REALISTIC TEST CASE  
 @ 24V, HALF THAT



DO NOT DESIGN TEST EQUIPMENT A CERTAIN WAY JUST BECAUSE IT'S EASY. MUST BE REALISTIC.

25 APR 13; Roderick.

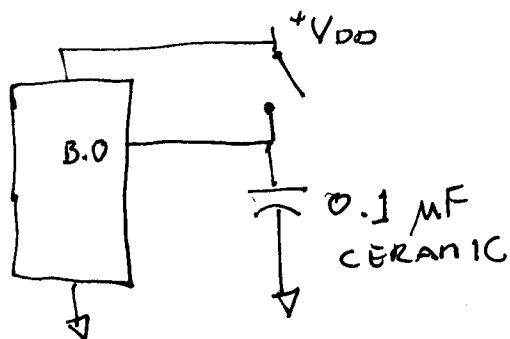DETERMINE MINIMUM INPUT IMPEDANCE OF PILAXE ADC.



WROTE PROGRAM TO MONITOR VOLTAGE ON CAPACITOR. READ ADC10 EVERY SECOND.

ASSUME DECAY IS  $V = V_0 e^{-t/RC}$


V STARTS AT 1023, MEASURE ELAPSED TIME TO DROP FROM 1022 TO 646  $\leftarrow (1023 \cdot e^{-1})$ . MEASURED  $t = 1877$  SEC.

$RC = 1877$   $C = 0.1 \mu F$  (PROBABLY A LITTLE MORE, IT WAS NOT A TIMING CAP)

$$R = 1877 / 10^{-7} = \text{ABOUT } 19 \times 10^9 = 19 \text{ G}\Omega$$

EVEN IF CAP IS +80%, THAT'S STILL  $\sim 10 \text{ G}\Omega$  NOT COUNTING ANY SELF-DISCHARGE.

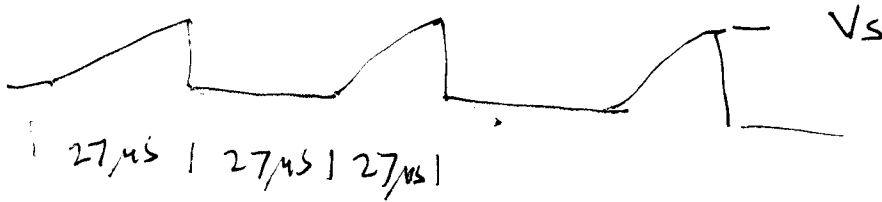THAT MEANS I CAN USE 100 K $\Omega$  SOURCE IMPEDANCE W/ CONFIDENCE, MAYBE EVEN 1 M $\Omega$ . NOISE IS ONLY




$R_s$  MUST BE SMALL, HAVE ~~OR~~ 0.05Ω, LOW OR POWER DISSIPATION WOULD BE HUGE. RESISTORS.  
 94 @ HALTED.

⊙ 40A, MEANS 200mV ACROSS RESISTOR.

$P = 8W$  IF CONSTANT. ~~AVERAGE POWER = 2W~~

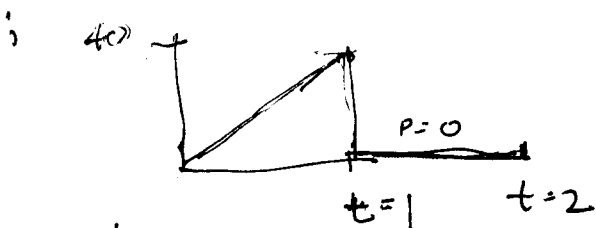RMS POWER = ~~EVERLASTING~~  
 $2.7W / 2 = 1.4W$   
 $i = kt$



$$P = \int_0^t i^2 R dt$$

$$i = 40t$$

$$= \int_0^1 (40t)^2 R dt$$

$$= 1600 \frac{t^3}{3} \cdot R = \frac{1600}{3} R = \frac{1}{3} \text{ OF PEAK POWER}$$

$$\int_0^t i^2 R dt$$

$$= k^2 \frac{j^3}{3} R t$$

$$= i^2 R \cdot \frac{k^2 j^3}{3}$$

FINAL

1.4W - COULD USE 2W OR 5W CURRENT SENSE

TEST EQY SETUP

